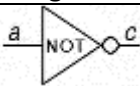
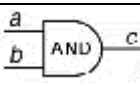
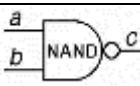
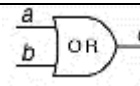
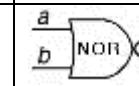
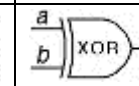


1. Analog vs. digital

- a. Analog – represent values by a continuously variable physical quantity
 - i. Here, voltage
 - ii. Key word is *continuous*
 - iii. Suited to amplification of real world phenomena (sound)
 - iv. Suited to calculating continuous function values (integrals)
 - v. Subject to noise, difficult to debug
- b. Digital – use discrete (discontinuous) values to represent data
 - i. Suited to discrete mathematics (like accounting)
 - ii. Needs to sample continuous data
 1. Will miss data that fluctuates faster than sampling rate
 - iii. Fixed 0 and 1, low and high, false and true
 - iv. Far more resistant to noise, easier to debug

2. Boolean algebra

- a. Algebra of truth values 0 and 1, along with conjunction (AND), disjunction (OR), and negation
 - i. George Boole, 1854
 - ii. Claude Shannon, 1938, uses it to solve circuit design problems
- b. $*$ = AND, $+$ = OR, \sim = negation, \oplus = XOR, variables A, B...
- c. Duality principle – swap all signs ($+$, $*$, 0, 1) and the underlying logic is still the same
- d. Operator precedence: NOT, AND, OR
- e. Logic types
 - i. Combinational – output based solely on current input
 - ii. Sequential logic – output based on input and previous stored values (memory)

Truth Tables for Digital Design Gates								
Operation:		Negation		AND	NAND	OR	NOR	XOR
Gates:								
A	B	$\sim A$	$\sim B$	$A * B$	$\sim(A * B)$	$A + B$	$\sim(A + B)$	$A \oplus B$
0	0	1	1	0	1	0	1	0
0	1	1	0	0	1	1	0	1
1	0	0	1	0	1	1	0	1
1	1	0	0	1	0	1	0	0

3. Logical equivalence

Laws of Logical Equivalence		
Name	OR version	AND version
<i>Commutative</i>	$A + B = B + A$	$A * B = B * A$
<i>Associative</i>	$(A + B) + C = A + (B + C)$	$(A * B) * C = A * (B * C)$
<i>Distributive</i>	$A + (B * C) = (A + B) * (A + C)$	$A * (B + C) = (A * B) + (A * C)$
<i>Idempotent</i>	$A + A = A$	$A * A = A$
<i>Identity</i>	$A + 0 = A$	$A * 1 = A$
	$A + 1 = 1$	$A * 0 = 0$
<i>Complement</i>	$A + \sim A = 1$	$A * \sim A = 0$
	$\sim 1 = 0$	$\sim 0 = 1$
<i>Double Negative</i>	$\sim(\sim A) = A$	
<i>De Morgan's</i>	$\sim(A + B) = \sim A * \sim B$	$\sim(A * B) = \sim A + \sim B$
<i>Absorption</i>	$A + (A * B) = A$	$A * (A + B) = A$

4. Examples


- a. $A + \sim A * B = A + B$. Why?

Assertion	Reason
$A + \sim A * B$	Initial function
$= (A + \sim A) * (A + B)$	Distributive Law for OR
$= 1 * (A + B)$	Complement Law for OR
$= (A + B) * 1$	Commutative Law for AND (won't bother with this from now on)
$= A + B$	Identity Law for AND

- b. Prove the OR version of the Absorption Law, $A + A * B = A$.

Assertion	Reason
$A + A * B$	Initial function
$= (A * 1) + (A * B)$	Identity Law for AND
$= A * (1 + B)$	Distributive Law for AND
$= A * (1)$	Identity Law for OR
$= A$	Identity Law for AND

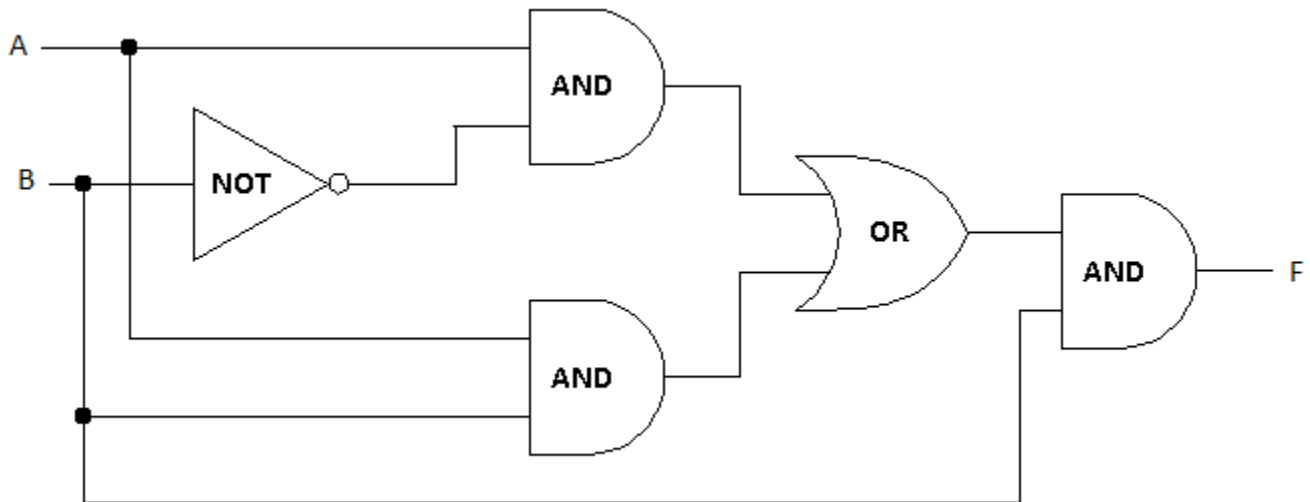c. Simplify the following digital logic circuit using propositional algebra.



Assertion	Reason
$f = ((A * \sim B) + (A * B)) * B$	Initial circuit logic
$= (A * (\sim B + B)) * B$	Distributive Law for OR
$= (A * 1) * B$	Complement Law for OR
$= A * B$	Identity Law for AND