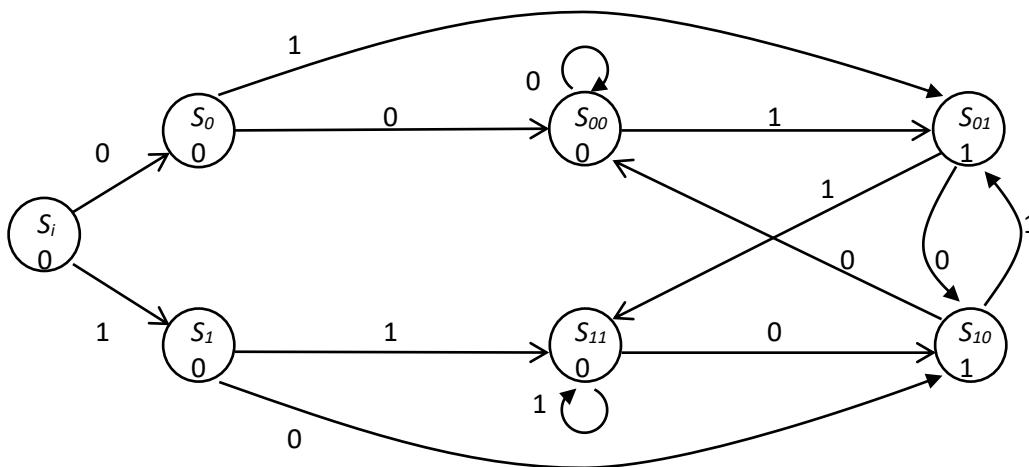


1. Recap of FSM design steps
 - a. Turn a word description into a state diagram
 - b. Turn the state diagram into a transition table
 - c. Use transition table to make K-maps to simplify circuit
 - d. Implement simplified circuit
2. Our word problem
 - a. Want to create an edge detecting circuit
 - b. Edge – position in a string of 0s and 1s where a 0 is adjacent to a 1
 - c. Essentially, XOR of adjacent bits
 - d. Since this involves remembering the previous value, machine will have different states
3. State transition diagram to minimize the number of states
 - a. Convert word description
 - i. States based on patterns of inputs
 - ii. Transitions between states based on individual input values
 - b. For this problem
 - i. S_i is our start state
 - ii. Every other state is labeled S_{xy} where x is the previous bit, y is the current bit
 1. Each state will have a unique label
 2. This minimizes the number of states
 - iii. Values inside each state are the output of the circuit
 1. 0 indicates no edge
 2. 1 indicates an edge was detected



- iv. Mealy model differences
 1. Mealy model state diagrams look slightly different
 - a. Outputs are on the edges/transitions between states, rather than the states themselves
 - b. Usually, the number before the slash indicates the input
 - c. Number after the slash indicates the output
 - d. Will come back to this later

4. State table

- Table that lists all transitions from each *present state* to the *next state* for different values of inputs
- Output z is specified with respect to the present state
- x is the next input

Present State	Next State		Output z
	$x = 0$	$x = 1$	
<i>i</i>	0	1	0
0	00	01	0
1	10	11	0
00	00	01	0
01	10	11	1
10	00	01	1
11	10	11	0

- Choice of flip-flops
 - Here, will keep it simple and use DFFs
 - Could use more complicated FFs, like J-K
 - Using these means more logic in front of FFs

5. Derivation of next-state and output expressions

- Will use a Moore model for this example
- Need to assign binary codes to each state
 - Since we have 7 states, will need 3 DFFs to represent all possible states
 - A, B, and C will represent the present state of the corresponding flip-flops
 - Initial state we start out in *i* must always be assigned to binary code of all 0s
 - Flip flops are assumed to be 0 when we first start circuit

Present State	Binary Code	Present State			Input x	Next State			Output z
		<i>A</i>	<i>B</i>	<i>C</i>		<i>A'</i>	<i>B'</i>	<i>C'</i>	
<i>i</i>	000	0	0	0	0	0	0	1	0
<i>i</i>	000	0	0	0	1	0	1	0	0
0	001	0	0	1	0	0	1	1	0
0	001	0	0	1	1	1	0	0	0
1	010	0	1	0	0	1	0	1	0
1	010	0	1	0	1	1	1	0	0
00	011	0	1	1	0	0	1	1	0
00	011	0	1	1	1	1	0	0	0
01	100	1	0	0	0	1	0	1	1
01	100	1	0	0	1	1	1	0	1
10	101	1	0	1	0	0	1	1	1
10	101	1	0	1	1	1	0	0	1
11	110	1	1	0	0	1	0	1	0
11	110	1	1	0	1	1	1	0	0