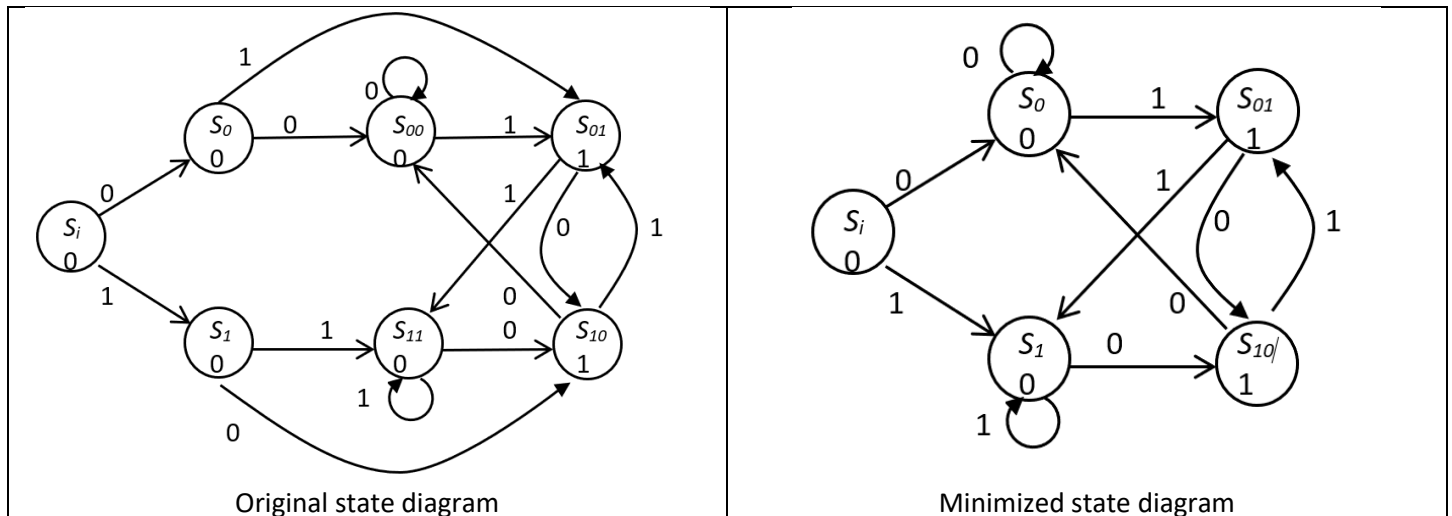


2. Mealy model versus Moore

- a. In general, Mealy model usually involves less circuitry
 - i. In this case, it does
 - ii. Only need two DFFs to remember previous bit
 - iii. XOR those values with input to give final output

3. Minimization

- a. Did the 7-state Moore model edge detector earlier
- b. Can minimize this down to 5 states, as shown below



c. Some definitions

- i. Two states S_i and S_j are *equivalent* if and only if for every possible input sequence, the same output sequence will be produced, regardless of whether S_i or S_j is the initial state
- ii. A *successor* to state S_i is a state that it transitions to based on its input
 1. S_0 in the unminimized FSM has S_{00} and S_{01} as its successors
 2. Differentiate successors based on input
 - a. S_{00} is the 0-successor of S_0
 - b. S_{01} is the 1-successor of S_0
 - c. Collectively, all immediate successors of a state form the *k-successors* of the state
- iii. A *block* is a subset of states that may be equivalent
- iv. A *partition* is a set of blocks where the states in each block are not equivalent to the states in the other blocks

4. Partition minimization procedure

- a. Will use the unminimized edge detector FSM for the rest of this example
- b. Start with all states in one partition and in same block
 - i. $P_1 = (S_i, S_0, S_1, S_{00}, S_{01}, S_{10}, S_{11})$
- c. Create P_2 by dividing states in P_1 that have same outputs
 - i. From definition of *equivalent*, states that have different outputs cannot be equivalent
 - ii. $P_2 = (S_i, S_0, S_1, S_{00}, S_{11}) (S_{01}, S_{10})$
- d. Create P_3 by looking at k-successors of each state
 - i. States of a block that have k-successors that are in different blocks from others in the block must be placed in new blocks, grouped by their shared k-successors

- ii. Look at first block $(S_i, S_0, S_1, S_{00}, S_{11})$
 - 1. 0-successors for the $(S_i, S_0, S_1, S_{00}, S_{11})$ block of P_2 are $S_0, S_{00}, S_{10}, S_{00}, S_{10}$, respectively
 - a. Need to divide states into those that stay in the block, and those that move to the (S_{01}, S_{10}) of P_2
 - b. Thus, we get (S_i, S_0, S_{00}) and (S_1, S_{11}) .
 - 2. 1-successors for (S_i, S_0, S_{00}) are S_1, S_{01}, S_{01} , respectively
 - a. So, we divide into (S_i) and (S_0, S_{00}) .
 - 3. 1-successors for (S_1, S_{11}) are S_{11}, S_{11} , so it will not need to be divided.
 - 4. First block of P_2 will be divided into the three blocks (S_i) , (S_1, S_{11}) and (S_0, S_{00}) in P_3 .
- iii. Now look at second block (S_{01}, S_{10})
 - 1. 0-successors for the (S_{01}, S_{10}) block of P_2 are S_{10}, S_{00} , respectively
 - 2. These are in different blocks from each other in P_2
 - 3. Will have to divide into two separate blocks (S_{01}) , and (S_{10})
- iv. So $P_3 = (S_i)(S_1, S_{11})(S_0, S_{00})(S_{01})(S_{10})$
- e. Further partitions
 - i. Once a block has one state in it, don't need to partition it further
 - 1. Will still need to use it to determine k-successors, though
 - ii. P_4 and further partitions look at each multiple-element block of the previous partition to see if the k-successors of its elements lead to the same blocks of the previous partition
 - 1. If not, the block must be further divided
 - 2. If any block splits, then we must continue to another step of partitioning
 - 3. If no block splits, then we are done
 - iii. Look at P_4 now
 - 1. 0-successors of (S_1, S_{11}) are both block (S_{10}) , so that will not cause the block to split.
 - 2. 1-successors are both (S_1, S_{11}) , so there is no need to separate the block further during this partitioning step
 - 3. 0-successors of (S_0, S_{00}) are both block (S_0, S_{00}) , so that will not cause the block to split
 - 4. 1-successors are both (S_{01}) , so there is no need to separate the block further during this partitioning step
 - iv. Since no block split, the final minimized partition is $P_3 = (S_i)(S_1, S_{11})(S_0, S_{00})(S_{01})(S_{10})$
 - 1. This matches the five-state minimized state diagram