
 


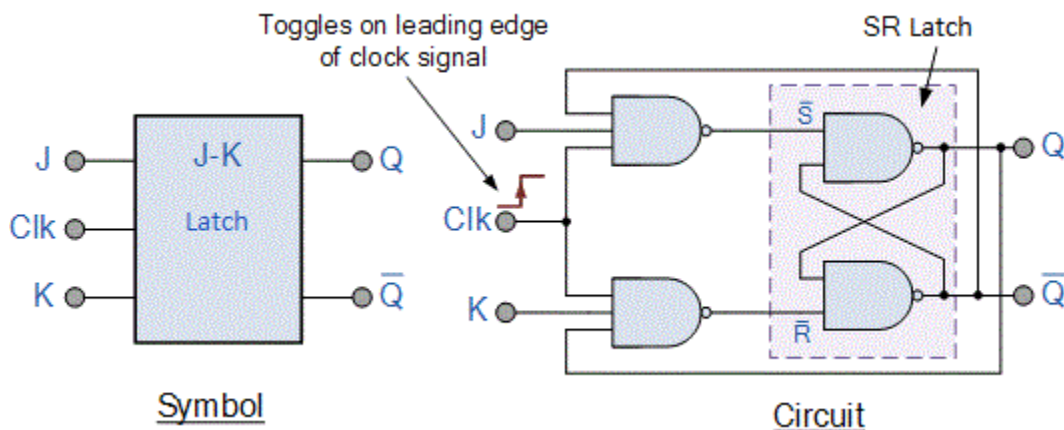
1. More on latches
 - a. Clocking the latches
 - i. Prevent the latch from changing, except at specific times as determined by the clock



2. Clocked J-K latch
 - a. Like a S-R latch, except that passing in $(S, R) = (1, 1)$ toggles/inverts Q instead of leading to undefined behavior
 - b. Uses feedback from outputs to do so










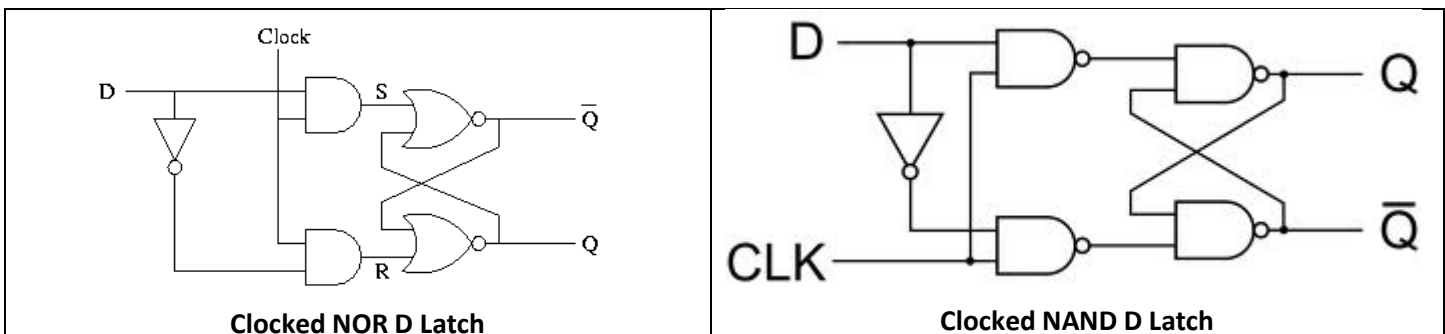
3. Clocked D latch
 - a. Only takes one input, ensures that inputs that cause unpredictable states don't occur
 - b. Output of latch is equal to the most recent value applied to the input
 - i. When clock is 1, sample the current value of D
 - ii. Store that value in the latch
 - iii. Can retrieve the value at output Q



4. Flip-flops
 - a. Circuit terminology

- i. Level sensitive – output controlled by the level of the clock input
- ii. Edge triggered – output changes only when the clock changes from one value to the other
 1. Positive / rising edge – when clock “rises” from 0 to 1
 2. Negative / falling edge – when clock “falls” from 1 to 0
- b. Back to flip-flops
 - i. Clocked (gated) latches are level sensitive
 - ii. Unlike latches, flip flops are edge-triggered
 - iii. Named so because they flip and flop from one stable state (0) to another (1)
- c. Advantages
 - i. Signal on input pin captured as soon as the clock changes
 - ii. Subsequent changes of the input are ignored until clock changes again
 - iii. Better timing control on complex circuits
- d. Types of flip flops

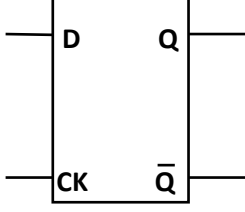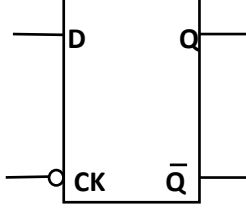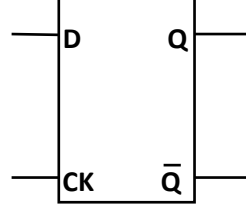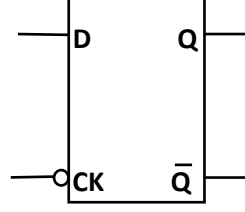			
Positive D Latch	Negative D Latch	Rising Edge D Flip-Flop	Falling Edge D Flip-Flop
Can change when the clock is high.	Can change when the clock is low.	Can change when clock goes from 0 to 1.	Can change when clock goes from 1 to 0.

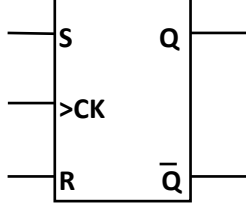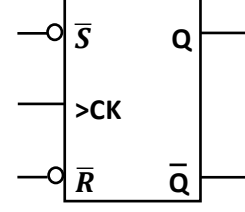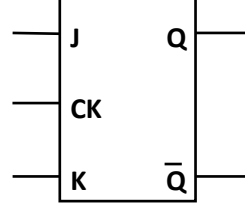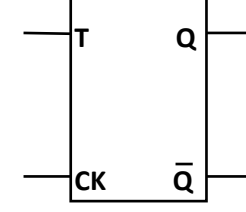																																																						
S-R Flip-Flop (NOR)	S-R Flip-Flop (NAND)	J-K Flip-Flop	T Flip-Flop																																																			
<table><tr><th>S</th><th>R</th><th>$Q(t+1)$</th></tr><tr><td>0</td><td>0</td><td>$Q(t)$</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>Undefined</td></tr></table>	S	R	$Q(t+1)$	0	0	$Q(t)$	0	1	0	1	0	1	1	1	Undefined	<table><tr><th>S</th><th>R</th><th>$Q(t+1)$</th></tr><tr><td>0</td><td>0</td><td>Undefined</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>$Q(t)$</td></tr></table>	S	R	$Q(t+1)$	0	0	Undefined	0	1	1	1	0	0	1	1	$Q(t)$	<table><tr><th>J</th><th>K</th><th>$Q(t+1)$</th></tr><tr><td>0</td><td>0</td><td>$Q(t)$</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>$\bar{Q}(t)$</td></tr></table>	J	K	$Q(t+1)$	0	0	$Q(t)$	0	1	0	1	0	1	1	1	$\bar{Q}(t)$	<table><tr><th>T</th><th>$Q(t+1)$</th></tr><tr><td>0</td><td>$Q(t)$</td></tr><tr><td>1</td><td>$\bar{Q}(t)$</td></tr></table>	T	$Q(t+1)$	0	$Q(t)$	1	$\bar{Q}(t)$
S	R	$Q(t+1)$																																																				
0	0	$Q(t)$																																																				
0	1	0																																																				
1	0	1																																																				
1	1	Undefined																																																				
S	R	$Q(t+1)$																																																				
0	0	Undefined																																																				
0	1	1																																																				
1	0	0																																																				
1	1	$Q(t)$																																																				
J	K	$Q(t+1)$																																																				
0	0	$Q(t)$																																																				
0	1	0																																																				
1	0	1																																																				
1	1	$\bar{Q}(t)$																																																				
T	$Q(t+1)$																																																					
0	$Q(t)$																																																					
1	$\bar{Q}(t)$																																																					

- e. Named flip flops work similarly to their latch counterparts
 - i. One new addition – T flip flop
 - ii. When T is high, on next clock the output is “toggled” and is inverted
 - iii. Same as (1, 1) input on J-K flip flop and latch


5. Flip flop timing

- a. Setup time t_{su} – minimum time before clock arrives that inputs must be stable and unchanging to ensure first latch in flip flop is stable
- b. Hold time t_h – minimum time after clock arrives that inputs must remain stable and unchanging to ensure first latch clock NAND is off
 - i. Not important for this course, but exists

6. Falling-edge Triggered Master-Slave D flip-flop


- a. Master latch in front controls slave latch’s output in back

b. Q_m is the output of the master latch

 


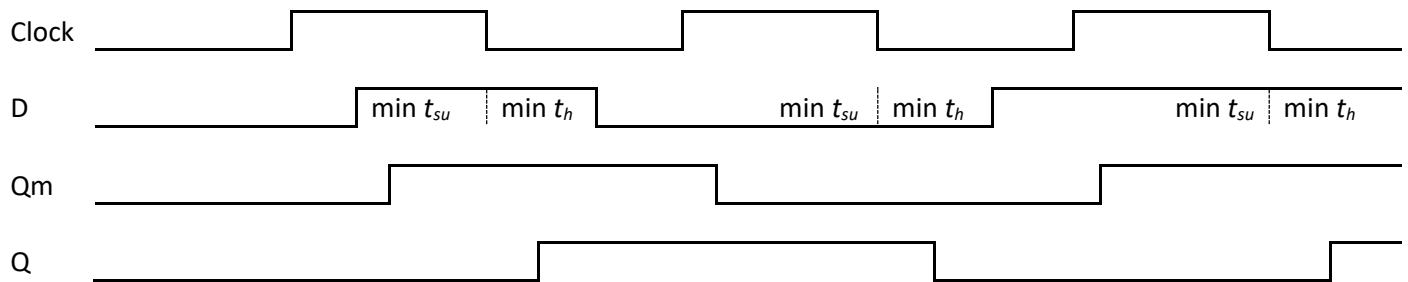
c. Timing diagram

- Remember that this flip flop is falling edge triggered
- In general, will stick to rising edge
- Input needs to stay constant before the falling edge for time t_{su}
- Input needs to stay constant after the falling edge for time t_h



7. Rising-edge triggered D flip-flop

  a. Here, t_h and t_{su} not specified explicitly but you can still see the impact on D



b. The second stage can be thought of as an S-R latch made of NANDs